

P.V.G.'s
Muktangan English School & Jr. College, Pune - 9
Annual Examination (2024-25)
STD XI

Subject : Computer Science (Paper II)
Date : 04.04.2025

Marks - 50
Time : - 8.30 - 11.30 am

Q1. A) Select the correct alternative and rewrite the sentences (4)

- 1) To inter connect the PC with telephone line _____ is necessary.
a) scanner b) Controller
c) modem d) printer
- 2) _____ is a volatile memory.
a) RAM b) PROM
c) ROM d) ESQARE PROM
- 3) When all inputs are low only then output is low this is the logic of _____ gate.
a) OR gate b) AND gate
c) NOT gate d) EX OR gate.
- 4) CMOS family is a _____ family.
a) bipolar b) unipolar
c) n polar d) none of the above

B) Answer the following (Any two) (6)

- 1) Explain charging and discharging of a capacitor.
- 2) Explain half adder with its true table.
- 3) Explain the uses of modem.

Q 2. A) Answer the following (Any two) (6)

- 1) State and prove D-Morgan's theorem.
- 2) State different types of semiconductor memory and explain any two.
- 3) What is Flip-Flop? State different types with their symbols and truth table.

B) Answer the following (Any one) (4)

- 1) Explain the construction of paper capacitor.
- 2) Define a) propagation delay
 b) fan-in / fan-out

Q3. A) Answer the following (Any two) (6)

- 1) Explain the construction of transistor and state its types.
- 2) Explain the basic gates with definition symbol and truth table.
- 3) Write the difference between MUX and DEMUX.

B) Answer the following (Any one) (4)

- 1) State different types of system bus and explain any two.
- 2) Write the advantages and disadvantages of floppy disk.

Q4. A) Answer the following (Any two) (6)

- 1) Explain the types of capacitor and explain any one of them in detail.
- 2) Explain the difference between volatile and non volatile memories. Give one example.
- 3) Define RC time constant.

B) Answer the following (Any one) (4)

1. Explain the concept of SMPS along with its advantages and disadvantages.
2. Draw logic diagram of J-K flip flop and explain it along its truth table.

Q5. A) Answer the following (Any two) (10)

- 1) Find RC time constant. If $R = 100 \text{ K}\Omega$ and $C = 100 \mu\text{f}$
- 2) A transformer has turns ratio of 5:1 and if secondary voltage is 40 V/50 Hz. Find the primary voltage and frequency of supply.
- 3) Find the value of carbon resistors by using colour code method.
 - a) Brown, Black, Orange, Silver.
 - b) Green, Black, Yellow, Silver.

OR

Q5. A) Answer the following (Any two) (10)

1. Find the equivalent capacitance if three capacitors each of $12 \mu\text{f}$ are connected in series and if they are connected in parallel.
2. In a transistor circuit if emitter current is 10 mA and base current is 2mA find collector current, α and β .
3. Compare TTL with CMOS family.

